

\$6.00

CONTENTS

Volume 8 Number 5
1996

Erno Borbely
**A 15W SE Power Amp
With 6C33C-B** 1

Norman Koren
**Improved Vacuum-Tube
Models for SPICE
Simulations** 18

Alan Kimmel
**Direct-Coupled
Mu Stage** 30

Chris Wolf
**World Class
Fit and Finish** 36

Donald S. Jenkins
**Filament Power
And Performance
Of the 2A3** 42

Rickard Berglund
**Enhanced-Mode
Operation** 50

GLASS CASE 5

ASK GA 54

LETTERS 58

CLASSIFIEDS 67

AD INDEX 68


READING GLASS

Audio Amateur readers, no doubt, are aware of the design talents of Erno Borbely, who has contributed many high-quality amp designs to *Audio Amateur & Electronics* magazine. Now, the German author showcases his magic in these pages with a single-ended design (also available from the author as a kit)

to page 5



GLASS AUDIO

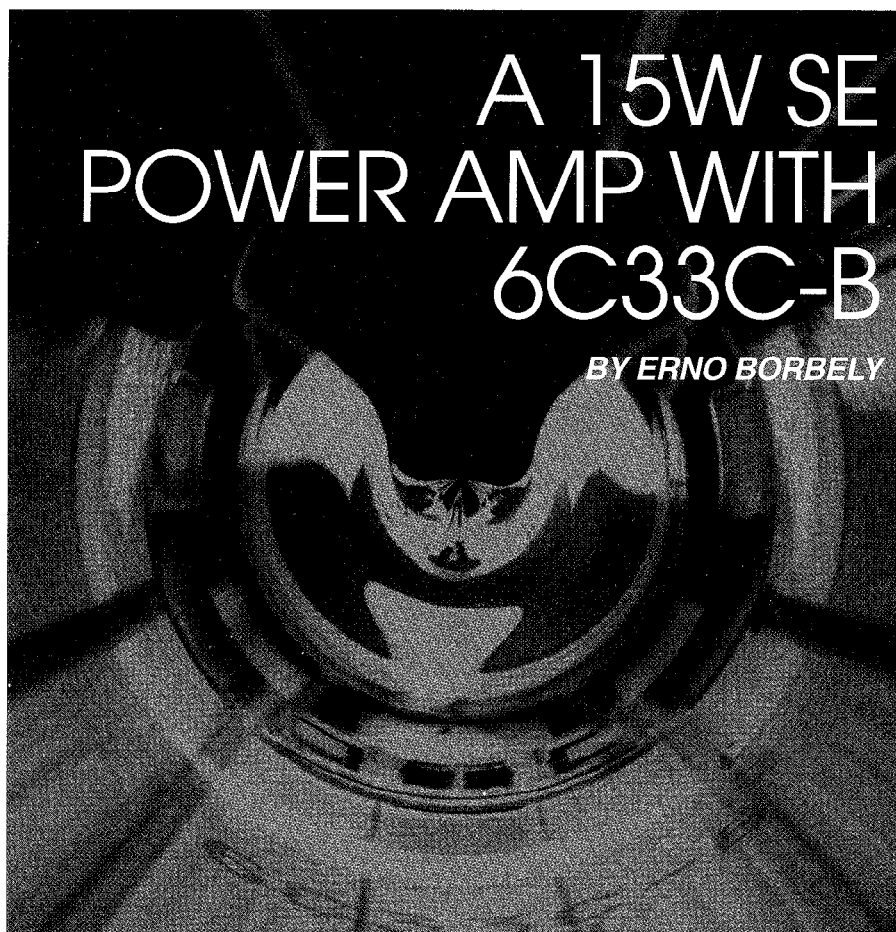

A 15W SE POWER AMP WITH 6C33C-B

BY ERNO BORBELY

I was not at all sure about getting into single-ended (SE) tube amps, because the choice of available tubes was limited. I do not like any of the high-efficiency speakers, and those with lower efficiency all require more than the meager 3W or 6-7W that the 2A3 or 300B SE amps, respectively, can deliver. Granted, there are 211s and 845s on the market that can drive just about anything, but, frankly, I am afraid of voltages higher than 350-400, and more than 1000V scares the hell out of me.

I have, however, found some interesting tubes that operate with reasonable voltages, among them the Russian 6C33C-B triode (*Photo 1*). Aside from its ability to deliver quite a lot more than the 2A3s, and to work off manageable supply voltages, it is also a work of art. Despite its consuming so much power that I can use it as a room heater on cold Bavarian winter nights, it inspires confidence because it is built like a battleship, with features found only in military gear, including thick glass and inter-

Continued on page 8

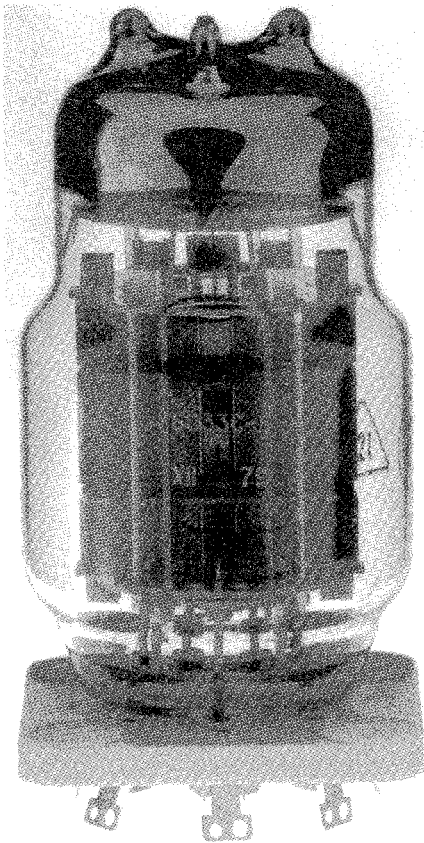


PHOTO 1: 6C33C-B tube.

from page 1

nal bracing to withstand vibrations. And the 15W certainly gives some hope that it can make less efficient speakers worth listening to.

The 6C33C-B Triode

Originally designed as a series element in voltage regulators for stationary and mobile equipment, the 6C33C-B is a large tube. Its greatest diameter is 65mm, and it is 130mm tall. It has two filaments and two cathodes. You can connect the two 6.3V/3.3A filaments in parallel or in series, consuming a total of 42W! Maximum anode dissipation is 45W with one cathode operating, and 60W with both.

The maximum anode voltage is 250V when the anode dissipation is more than 30W, and 450V when it's less than 30W. Due to the high filament and anode dissipation, the tube runs very hot (260°C), so you can use it only with ceramic sockets. You should also drill holes around the socket for increased ventilation.

The 6C33C-B has a transconductance of 39mA/V, a μ of less than 4, and a very low plate resistance of about 100Ω. The anode characteristics are shown in Fig. 1. Due to its unique characteristics, the tube is well suited for audio use, but you need to use transformers with pri-

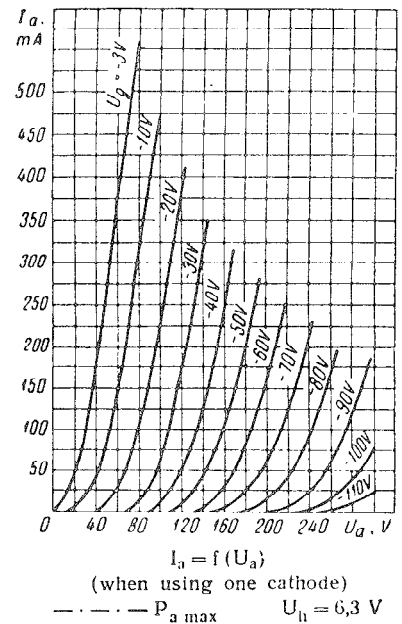
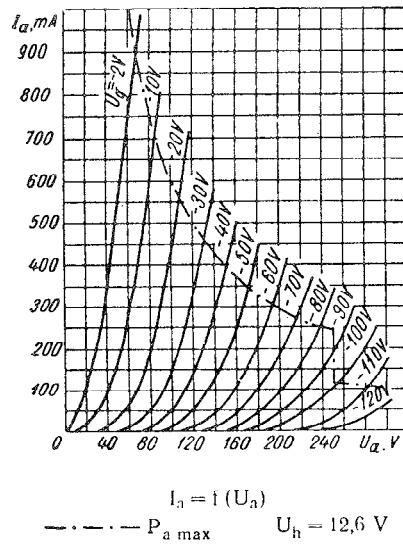


FIGURE 1: Anode characteristics of the 6C33C-B.

mary impedances that are much lower than conventional ones (Photo 2). In SE mode, the primary impedance of the transformer is about 600Ω; in push-pull amplifiers, it is 1-1.2kΩ.

Fixed Bias or Cathode Bias

The basic circuits for operating the 6C33C-B in SE mode with fixed bias and cathode bias are shown in Figs. 2a and 2b. Although the two circuits are similar in performance, the cathode-bias circuit requires a higher supply voltage, with approximately 15W dissipated in the cathode resistor, and it yields slightly less power and has worse distortion than the fixed-bias circuit. Its advantage is the simpler power supply, because you don't need a bias circuit.

I chose an anode voltage of about 200

and an anode current of 220mA for both circuits. Though I operate the 6C33C-B with both filaments (and consequently both cathodes), I selected an operating point that results in 44W anode dissipation. This is just a bit more than two-thirds of the maximum, thus ensuring longer tube life. With the 600Ω output transformer, this yields about 15W. If you wish to push the tube closer to its limits, you could probably get 18-20W output.

A Simple SE Amplifier

The 6C33C-B needs a very large voltage swing at the input to produce this output. Measurements show that approximately 55V RMS are needed to drive it. The simplest circuit that can produce such a voltage swing with reasonable distortion is shown in Fig. 3. Half of the

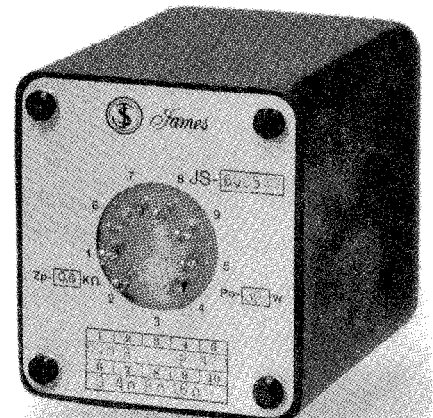
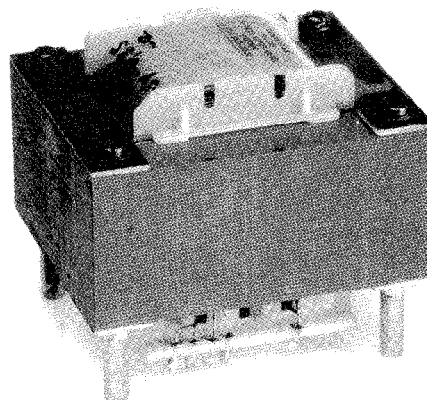


PHOTO 2: Two transformer prototypes for the 6C33C-B-based power amp: the open-frame transformer (left) by Johan Bernström of Sentec (Sweden) and the potted version by James Wu of Taiwan (right).

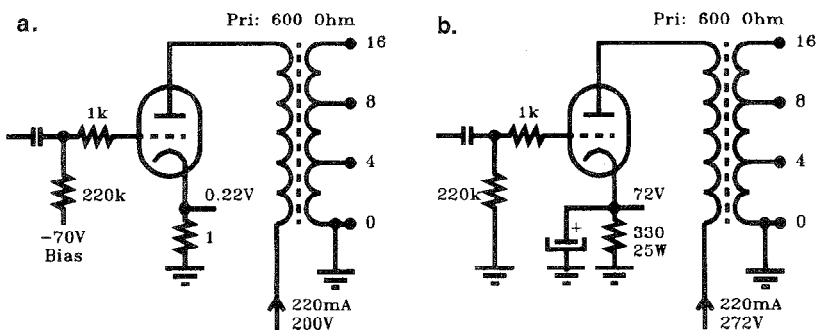


FIGURE 2: Basic circuits for the 6C33C-B in SE mode: a) fixed bias; b) cathode bias.

6SN7GT/6H8C is operated in grounded cathode configuration, while the other half is used as a cathode follower. The frequency response of the driver circuit is several hundred kHz. The gain is low, and it needs 3.5V RMS to drive the 6C33C-B. Table 1 shows distortion as a function of output voltage across an 8Ω load.

The distortion, which is predominantly second harmonic, is, as expected, not very impressive. But again, that is probably the very reason that some of you like the sound of the SE amplifiers. As far as I am concerned, I like tube sound, but I don't necessarily like the several percent of distortion of any kind. You can't use feedback, which would help to linearize the circuit, because it does not have enough open-loop gain.

Distortion Cancellation

Instead of feedback, I am using distortion cancellation¹ by permission of Johan Bernström of Sentec AB in Sweden, who

says that this technique is not used much nowadays, although it is ideal for SE amplifiers. A simple version of this is shown with dotted lines in Fig. 3.

The resistor and trimpot load the anode circuit of the 6SN7GT/6H8C and predistort the signal. Since this is 180°

DISTORTION MEASUREMENTS			
OUTPUT VOLTAGE ACROSS 8Ω	OUTPUT POWER INTO 8Ω	DISTORTION WITHOUT CANCELLATION	DISTORTION WITH CANCELLATION
1V RMS	0.125W	0.5%	0.15%
2V RMS	0.5W	1%	0.3%
4V RMS	2W	2%	0.8%
8V RMS	8W	4.2%	2%
10V RMS	12.5W	6.5%	3.5%
11V RMS	15.125W	10%	6%

out of phase with the 6C33C-B output, the distortion in the 6SN7GT/6H8C and the 6C33C-B tend to cancel each other. The distortion with cancellation is also shown in Table 1. Obviously, the cancellation is not 100%, but the distortion is significantly better than without it, especially at lower levels.

The output impedance of the amplifier, measured on the 8Ω output, is 2.8Ω;

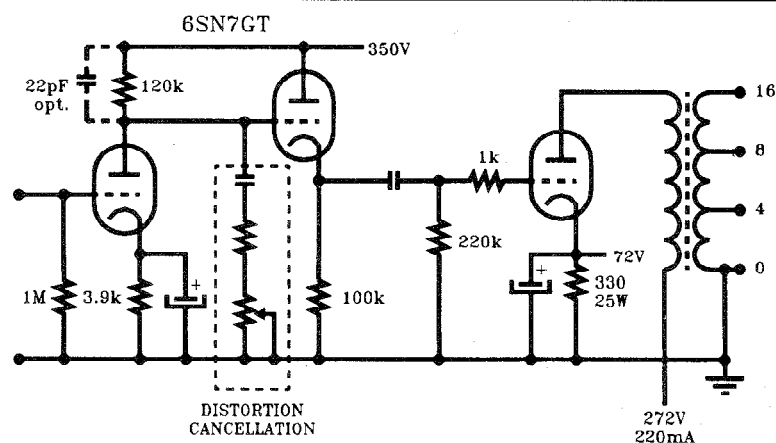


FIGURE 3: Simple SE power amplifier with cathode bias.

The Industry's Finest Connectors.

TIFE
ELECTRONICS COMPANY

TIFE Electronics Company • 44 Pearl Pentecost Road / Winder, GA 30680 • (770)867-6300 / 2713 (Fax)

Reader Service #52

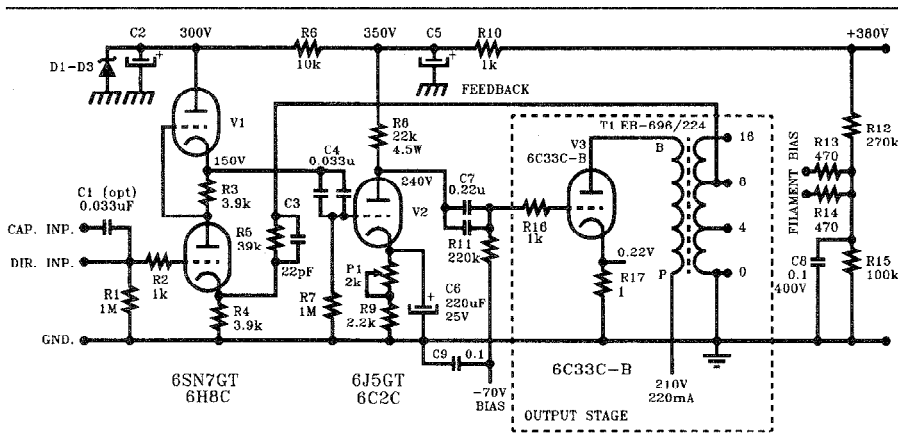


FIGURE 4: Amplifier with distortion cancellation and optional feedback.

TABLE 2

DISTORTION FROM FIG. 4

OUTPUT VOLTAGE ACROSS 8Ω	OUTPUT POWER INTO 8Ω	DISTORTION WITH BUILT-IN CANCELLATION	DISTORTION WITH OPTIONAL FEEDBACK
1V RMS	0.125W	0.06%	0.02%
2V RMS	0.5W	0.13%	0.043%
4V RMS	2W	0.38%	0.125%
8V RMS	8W	1.4%	0.48%
10V RMS	12.5W	2.2%	0.78%
11V RMS	15.125W	2.8%	1%
12V RMS	18W	3.3%	1.6%
13.5V RMS	22.7W	10%	10%

TABLE 3

PARTS LIST FOR 6C33C-B DRIVER BOARD EB-396/225

RESISTORS

R1, R7	1M
R2	1k
R3, R4	3.9k
R5	39k
R6	10k, 4.5W
R8	22k, 4.5W
R9	2.2k
R10	1k, 4.5W
R11	221k
R12	270k, 1.4W
R13, R14	470, 1.1W
R15	100k, 1.4W

All resistors 0.5W, 1% Metallfilm, or Tantalum, unless otherwise noted.

TRIMPOT

P1	2k, 0.5W	CERMET, ROE CT-9W
----	----------	-------------------

CAPACITORS

C1 (opt.)	0.033μF/400V	WIMA MKP-10
C2	10μF/450V	
C3	22pF/160V	PS
C4	0.033μF/400V	WIMA MKP-10 in parallel with Siemens PP
C5	47μF/450V	Siemens
C6	220μF/25V	ROE/FROLYT EKR
C7	0.22μF/400V	WIMA MKP-10 in parallel with Siemens PP
C8	0.1μF/400V	WIMA MKP-10
C9	0.1μF/160V	RIFA PP

TUBES, DIODES

V1	6SN7GT/6H8C
V2	6J5GT/6C2C
D1, D2, D3	100V, 1W zener

MISCELLANEOUS

20 × 1mm solder pins
PCB: EB-396/225
8-pin OCTAL Sockets

i.e., the damping factor is 2.85. This is very low, and the loudspeaker needs to have a constant impedance versus frequency, otherwise the overall frequency response will be nonlinear. Wideband loudspeakers will probably work very well with this high-output impedance, but complex, multiway speakers will have problems. You can reduce the output impedance by applying negative feedback around the amplifier. However, to apply feedback, you need more gain in the driver, and the simplest way to get it is to add a predriver.

Two-Stage Driver

Figure 4 shows a fixed-bias 6C33C-B amplifier with a two-stage driver, which can also be used with the cathode-bias output. The input stage is a series-connected 6SN7GT/6H8C with very good linearity and low output impedance. The latter is necessary because of the rather high input capacitance of the 6C33C-B.

The second stage is a grounded cathode amplifier with a 6J5GT/6C2C triode and built-in distortion cancellation. The principle is the same as described earlier, but this time you build the cancellation into the amplifier by changing the DC operating point of the 6J5GT tube. The adjustment requires a distortion analyzer and is done with P1. If you don't have one, replace the trimpot with a jumper. Distortion will not be as low as with the cancellation adjustment, but certainly will be close enough to work well.

You will notice that I have removed the cathode follower from the driver. I know that

TABLE 4

PARTS LIST FOR OUTPUT STAGE

RESISTORS

R16	1k
R17	1, 4.5W

TUBES

V3	6C33C-B
----	---------

TRANSFORMER

T1	EB-696/224
----	------------

MISCELLANEOUS

Tube socket for 6C33C-B

most published 6C33C-B circuits use a cathode follower to drive the 6C33C-B. Some of them even DC-couple the cathode follower to the 6C33C-B, which is, of course, necessary if you want to drive it with grid current. However, that was not my intention here; in fact, I wanted to prevent the 6C33C-B from going into that condition. On the other hand, it is true that the 6C33C-B has some input capacitance that has to be charged and discharged by the driver, but this can also be done with a grounded cathode amp, if it has enough current drive capability.

The distortion of the amplifier in Fig. 4 is shown in Table 2. It has been minimized at 4V RMS output. Again, the cancellation is not 100%, but now you have enough open-loop gain in the complete amplifier to apply a small amount of feedback around it and reduce the distortion further.

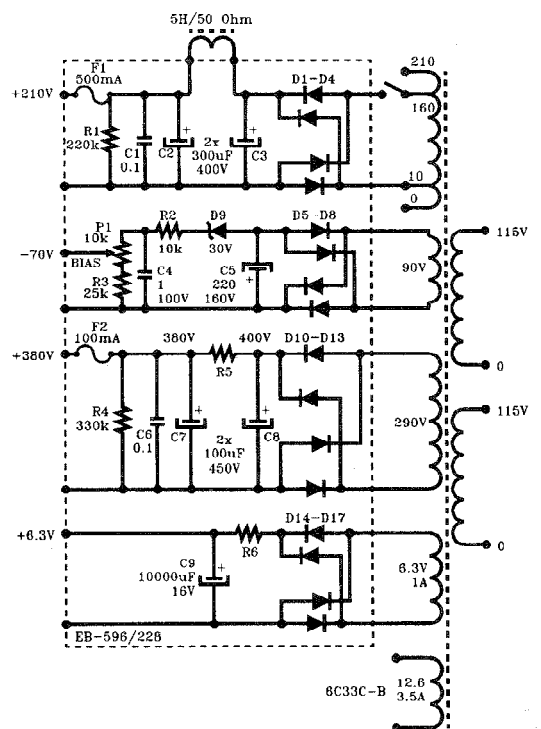


FIGURE 5: Power-supply schematic.

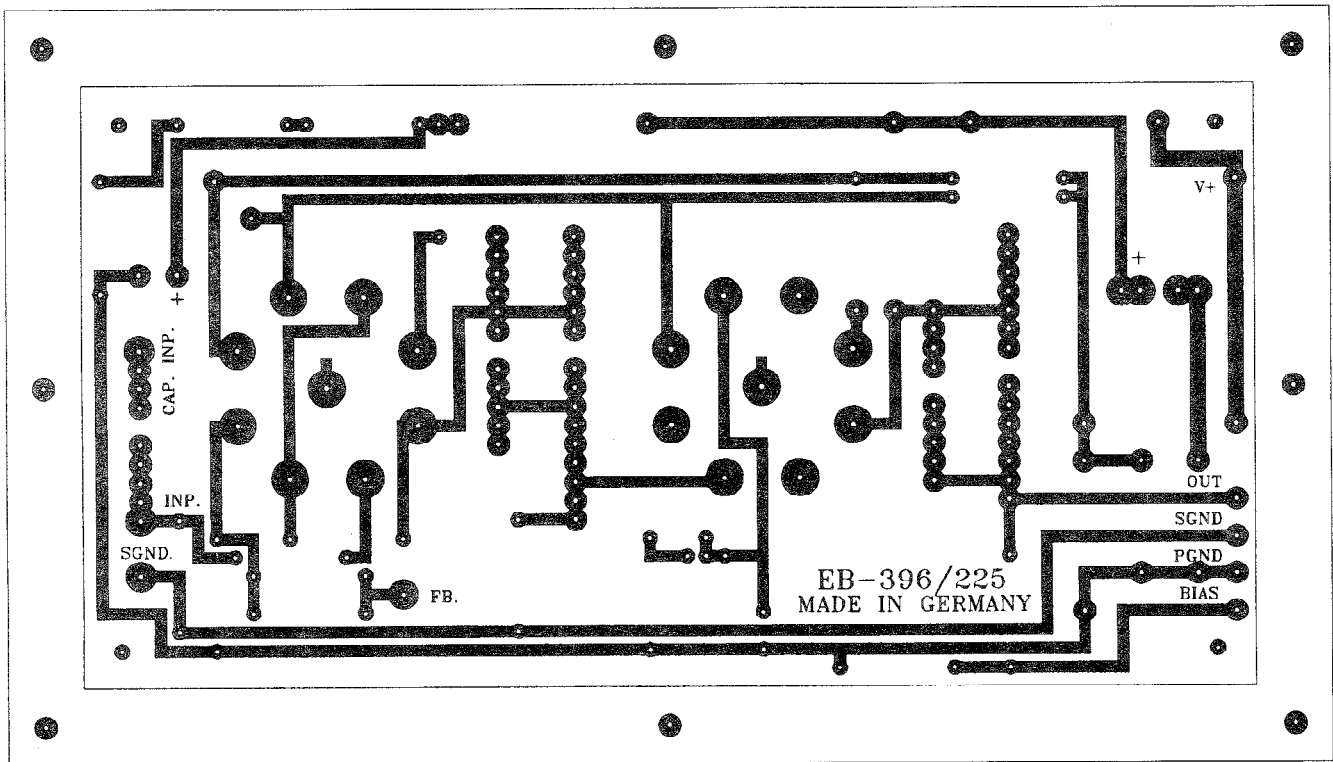


FIGURE 6: Driver for SE power amp (1:1).

Adding a Bit of Feedback

The maximum output of the amplifier with 10% THD has increased to over 20W. The open-loop gain is 23.1 times (27.3dB), and it now needs 0.476V RMS

to drive it to 15W. The output impedance has not changed with the two-stage driver circuit, but you can apply feedback to reduce it. The feedback is going from the 8Ω output to the cathode of the input stage.

-1dB at 100kHz. The amplifier's power bandwidth with the EB-696/224 transformer is 40Hz-20kHz without feedback.

Because of the wide bandwidth of the
to page 48

TABLE 5

PARTS LIST FOR POWER SUPPLY BOARD EB-596/228

RESISTORS		
R1	220k, 1.4W	Metal oxide
R2	10k, 0.5W	Metal film
R3	25k, 0.5W	Metal film
R4	330k, 1.4W	Metal oxide
R5	1k, 4.5W	Metal oxide
R6	0.22, 4.5W	Adj. for 6.3V.
TRIMPOT		
P1	10k, 0.5W	CERMET, ROE CT-9W
CAPACITORS		
C1, C6	0.1μF, 400V	WIMA MKP-10
C2, C3	300μF, 400V	Siemens
C4	1μF, 100V	ROE MKT-1826
C5	220μF, 160V	ROE EKO
C7, C8	100μF, 450V	Siemens
C9	10,000μF, 16V	Siemens
DIODES		
D1, D2, D3, D4	BYT13-1000	3A, 1kV
D5, D6, D7, D8	KB-10,	1.5A, 250V Bridge
D9		30V, 1W zener
D10, D11, D12, D13	BYT11-1000	1A, 1kV
D14, D15, D16, D17	11DQ10,	1.1A, 100V, Schottky
MISCELLANEOUS		
F1	Fuse holder Fuse: 500mA	Wickman, 19646 holder, 19648 cover Medium
F2	Fuse holder Fuse: 100 mA	Wickman, 19646 holder, 19648 cover Medium
40 × 1mm Solder pins		
PCB	EB-596/228	

As you now have an extra 180° phase shift in the chain, you must reverse the primary taps of the output transformer to get the right phase for the feedback. The feedback reduces the gain to about 7.3 times (17.3dB), so it is approximately 10dB. The input voltage is 1.5V RMS for 15W output.

The feedback has reduced the distortion further, as indicated in Table 2. The output impedance decreased to 0.6Ω, with a damping factor of 13.3 times, which is probably enough to work with most commercial speakers.

Rise time for the feedback amplifier is 4μs at 10V peak-to-peak output voltage. Frequency response without feedback is -3dB at 50kHz; with feedback, it increases to

The 6C33C-B KIT

The Borbely Audio Kit includes:

- 6C33C-B with grid and cathode resistors (2)
- Ceramic sockets for the 6C33C-B (2)
- EB-696/224 output transformers (2)
- 1 pair of EB-396/225 driver boards (two-stage driver as shown in Fig. 4)
- Optional: 1 pair of EB-596/228 power-supply boards (as shown in Fig. 5)

Specifications for the EB-696/224 output transformer (subject to change without notice):

- Power rating: 30W
- Primary imp.: 600Ω
- Secondary imp.: 4Ω, 8Ω
- Primary current: 0.4A
- Secondary current: 3A
- Frequency response: 20Hz: -1.5dB
50kHz: -2.7dB
- Weight: approximately 3kg.

Mains transformer, connectors, switches, etc., are not included in the kit; however, Borbely Audio can deliver these on request. Please send for a quote.

The 6C33C-B SE amplifier design with the EB-396/225 driver board, and the EB-596/228 power-supply board are the property of Erno Borbely/Borbely Audio. Commercial use is not authorized without a license agreement with Erno Borbely/Borbely Audio. Borbely Audio reserves the right to improve or otherwise alter any specification supplied in this document or any documentation supplied hereafter.

The
HARTSFIELD
 and **STUDIO**
STANDARD
 Full 3-way horn
 systems and the
STUDIO
MONITOR
 2-way system for
 truly lifelike
 sounds
 from your tube
 amplifiers.

Contact:

CLASSIC AUDIO
REPRODUCTIONS

for further information

(810) 229-5191


Reader Service #87

An enterprise specializing in audio products is using Directly Heated Triodes

Write:

Triode Music
 43 Wineva Ave.
 Toronto, On.
 Canada
 M4L 2T1

Email:
 vacuum
 @
 visinet.ca

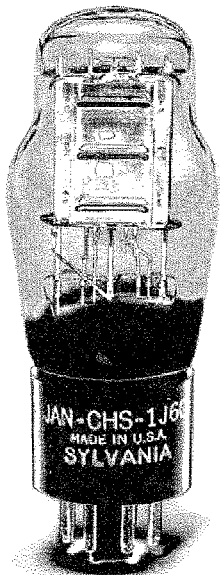

We now have available a 300B SE amplifier kit. Special efforts have been taken to make this amplifier a musical pleasure, while having technical accuracy. A minimalist front-end, higher load line, lower B+ and massive output transformer have been designed into this amplifier. All these features combine to give excellent articulation, a warm top-end, a solid bottom-end, and hours of listening pleasure. We also offer a special line of front-end gain modules for the convenience of amateur audio enthusiasts. The premier gain module uses a Directly Heated Triode for an incredible musical match for 2A3, 300B and 211 Single Ended amplifier designs. Three other conventional gain modules are available for low microphonic high gain requirements, with convenience and excellent sound.

Reader Service #72

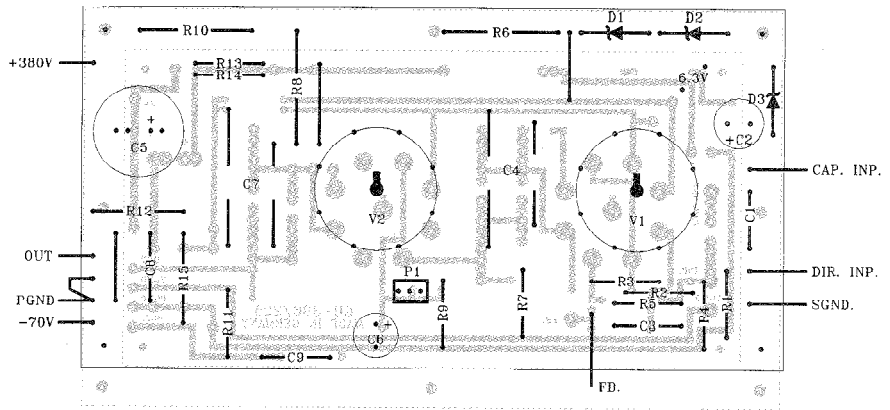


FIGURE 7: Stuffing guide for driver board.

from page 14

output transformer, it is easy to apply a small amount of feedback around the amp without instability problems. I urge you to experiment, both in terms of driver circuits and ways of reducing the inherent distortion in the SE output stage. Naturally, if you want to preserve the inherent distortion of the SE amplifier, you can remove the distortion-cancellation circuit and the feedback. Tables 3 and 4 are the parts lists for the driver board and output stage.

Power Supply

You can conceive of the power supply for this amplifier in many different

ways. Tube rectifiers for the output stage would probably cause too much voltage drop and are not recommended. Borbely Audio offers a power-supply board that provides two high-voltage rectifier sections, one for the output tube and one for the drivers. All diodes are fast/soft recovery types. The output tube is fed from a C-L-C filter, and the drivers from a C-R-C filter.

Since the 6C33C-B takes about two minutes to warm up, I have indicated a switch between the transformer and the supply, so that you can switch on the high voltage after two minutes. To the best of my knowledge, cathode stripping should not occur at the low voltage

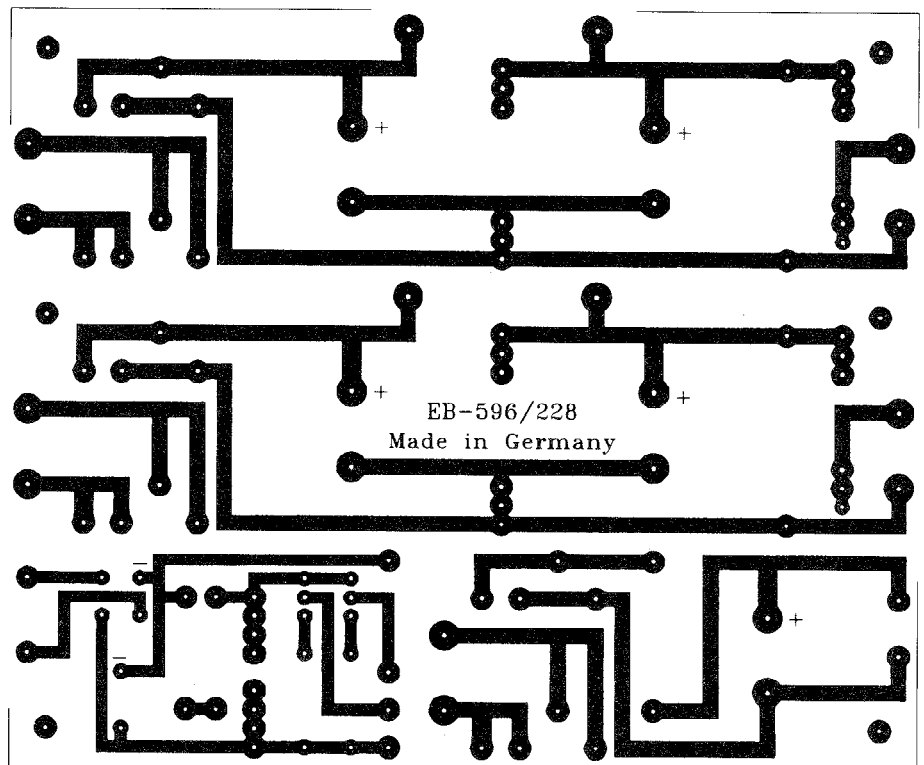


FIGURE 8: Power supply for tube amplifiers (1:1).

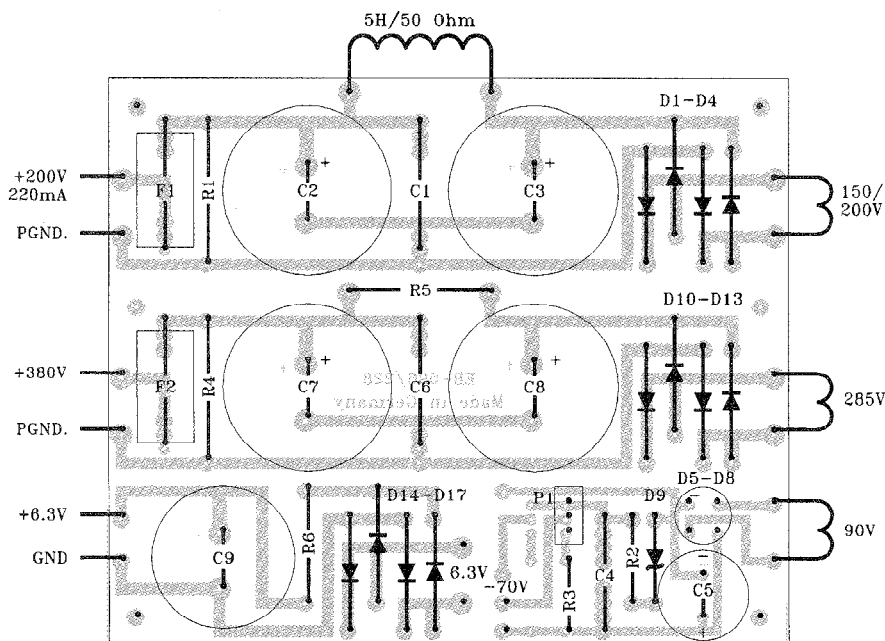


FIGURE 9: Stuffing guide for 6C33C-B power supply.

you are using here, but not knowing all the nitty-gritty of the 6C33C-B, it might be a good idea to exercise some caution. It is very important to have a well-filtered supply to avoid driver hum. Consequently, if you have a small choke in your jolly box, it is worth using it to replace the resistor in the driver power supply.

The driver tubes are heated with DC. A 3A bridge and a 10,000 μ F cap off the 6.3V will do it. Check the DC voltage on the tubes, and if it is more than 6.3V, connect a small resistor in series with the filter capacitor. The filaments are biased at approximately +100V on the driver board to avoid cathode-filament breakdown and to reduce hum. Alternatively, you can use one of the filament regulators offered by Borbely Audio.

Bias Compensation

The bias voltage, in case you choose to use fixed bias, should be present before you switch on the anode voltage. You can do this with a diode bridge and a capacitor. However, note that an increase in mains voltage causes a significant increase in the anode current if you keep the bias constant. To compen-

REFERENCES

1. The concepts of "distortion cancellation" and "bias compensation" are the intellectual property of Johan Bernström, Sentec AB, Sweden.

SOURCE

Borbely Audio
Melchior Fanger Strasse 34A
82205 Neu-Gilching
Germany

sate for this, you need to increase the bias faster—percentage wise—than the mains voltage is increasing.

Ideally, an increase in mains voltage should not cause any increase in the anode current. Practically speaking, the increase should be kept to, say, less than 20mA over a mains voltage increase of 20V. Again using an idea from Johan Bernström, you can do this with a zener diode in series with a resistor chain, as shown in Fig. 5. This circuit ensures that the anode current doesn't run away with an increase of the mains voltage. Table 5 shows the power-supply parts list.

Monoblocks

I recommend you build the 6C33C-B SE amplifier as a monoblock, which ensures short cables between the amp and the speaker and lets you optimize the power supply and the internal wiring. The wiring of the amplifier is partially point-to-point, in that the 6C33C-B has a chassis-mount socket and the grid and cathode resistors must be wired directly to the socket. The rest of the amplifier, including the power supplies, can also be hand-wired, or, as with the Borbely Audio Kits, can be made on PCBs. (Figures 6-9 show the driver and power-supply printed-circuit boards.)

Setup Procedure

The 6C33C-B SE amplifier requires very little setup. Obviously, you need to check all the voltages on the power supply and the driver board according to the schematics. Although the voltages

used in this amplifier are relatively low, I recommend exercising utmost caution when testing the circuits. If you have no experience with tube circuits, I recommend that you ask an experienced friend or an electronics technician to test your amplifier.

To make the distortion-cancellation adjustment, you need a distortion analyzer. Adjust the output to 4V RMS/1kHz across the 8 Ω load and measure the distortion. Adjust P1 slowly until you observe a dip in the distortion. Check the distortion at other levels, just to make sure the circuit is working properly. If you don't have a distortion analyzer, put a jumper in place of P1. No further adjustments are required. ♦

OF NOTE IN Speaker Builder

Issue 5, 1996

- True Bass
- Reflecting on Echoes and the Cepstrum
- The Convertible Monitor
- The Opposite Moduli (OM) Speaker Cabinet
- Software Review: Visual Ears

GO AHEAD

Ask top engineers and music lovers worldwide what capacitors they choose for their ultimate designs.

H O V L A N D

MUSICAP®

The most naturally revealing capacitor. Film and foil polypropylene construction - optimized for fine speakers and vacuum tube electronics. Precision made in the USA.

Values from .01 μ F to 10 μ F.

Listen and compare for yourself.

UPGRADE NOW

"If you want see-thru, high definition, detail and listenability, try the Musicaps."

Joe Roberts, SOUND PRACTICES, ISSUE 6

To order contact one of the following:

- Welborne Labs 303-470-6585
- The Parts Connection 800-769-0747
- A & S Speakers 510-685-5252
- Allpass Technologies, Inc. 407-786-0623
- Anchor Cross Co., Japan, 81-3-3203-5606
- SJS Electroacoustics, England 44-1706-823025
- Tang Hill International Ltd., 886-2-5813605
- OEMs contact Hovland Company at:
ph 209-966-4377 • fax 209-966-4632

Reader Service #60